

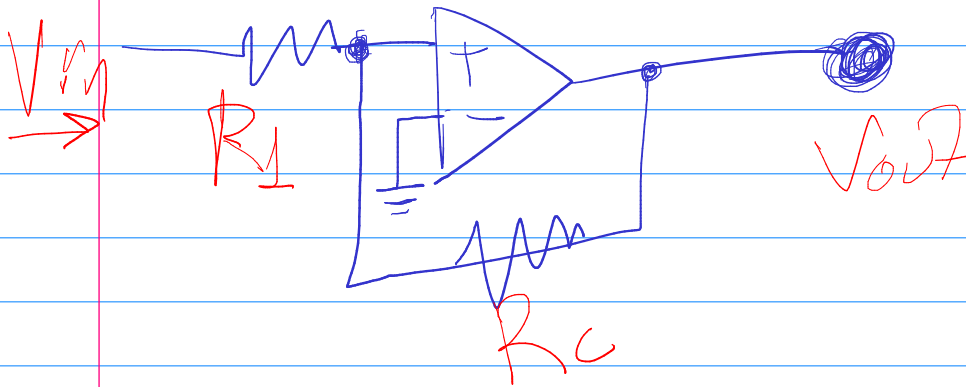
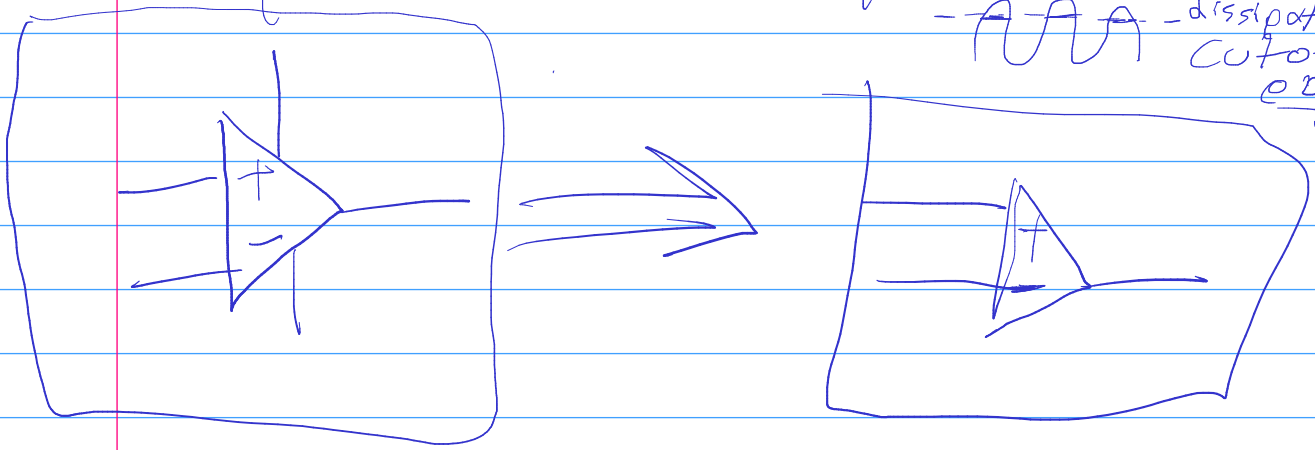


Operational Amplifiers

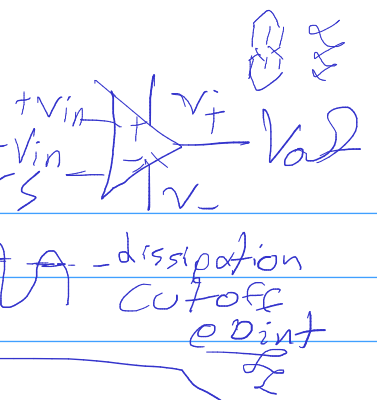

Non-Inverting Amp (?)

Case 1:
 $A_0 \rightarrow \infty$

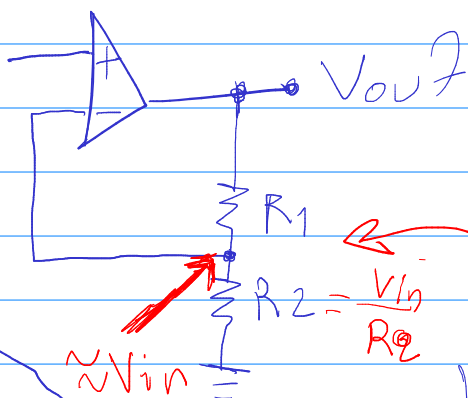

feedback goes to (-)
always (?)

fair enough?

$$V_{out} = (V_{in+} - V_{in-}) A_0$$

$V_{in+} \approx V_{in}$
 $V_{in-} \approx \frac{V_{in}}{R_2}$
finite
very small
very large

$$V_{out} = \frac{V_{in}}{R_2} (R_1 + R_2)$$

$I \cdot R_1 + R_2$

Voltage Gain:

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_1}{R_2}$$


Ground:

A point of reference for voltage. A deep for current.

Case 2: Do not very high

Voltage Divider:

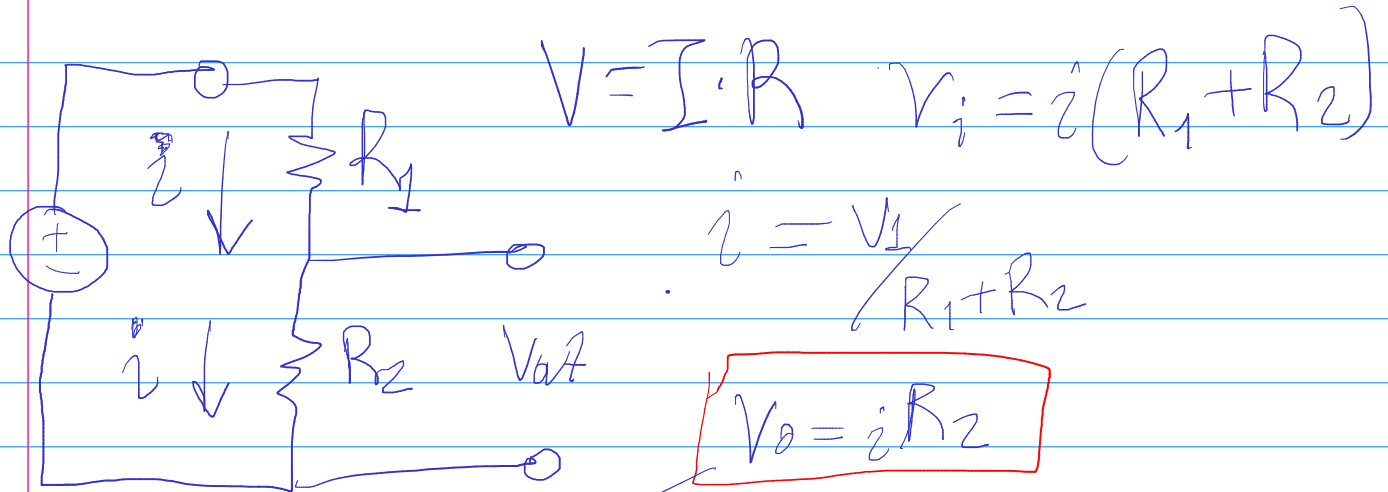Allows you to div the voltage between 2 resistors. Therefore allowing you to step down the voltage, from a power supply, to any other voltage you require.



$$i = \frac{V_o}{R_2}$$

proportion to V_{out}
proportion to R_2
MONO

Since: i is the same cause it's a series circuit & same everywhere so.

$$\frac{V_o}{R_2} = \frac{V_i}{R_1 + R_2} \Rightarrow V_{out} = \left(\frac{V_i}{R_1 + R_2} \right) \cdot R_2$$

IMPORTANT or $V_i = \frac{R_2}{R_1 + R_2}$